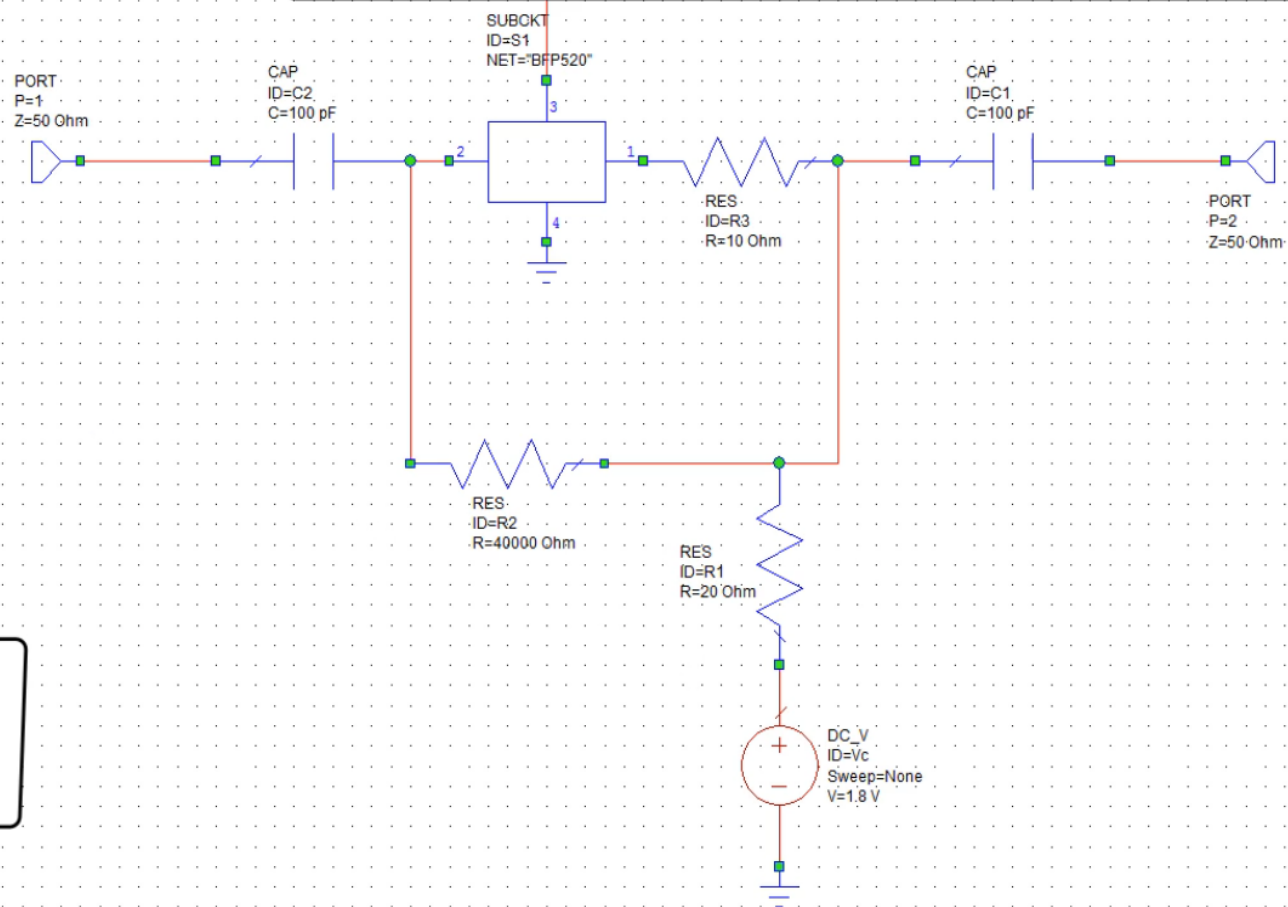


## Measure DC IV as annotation (drawn on the schematic):

RC on the schematic -> Add Annotation:  
DCIA for DC currents.  
DCVA for DC Voltages.

Simulate in order to see the annotations.



We can now replace the BIASTEE models with a non-ideal bias circuit.