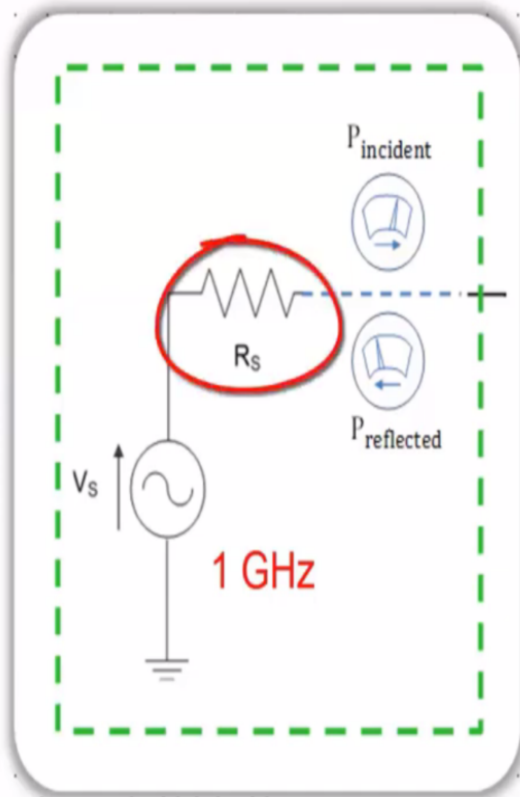



PORT
P=1
Z=50 Ohm



Rs is like Z=50 ohm and the port can measure diirectional power or called the reflection coefficient the Pin an pout



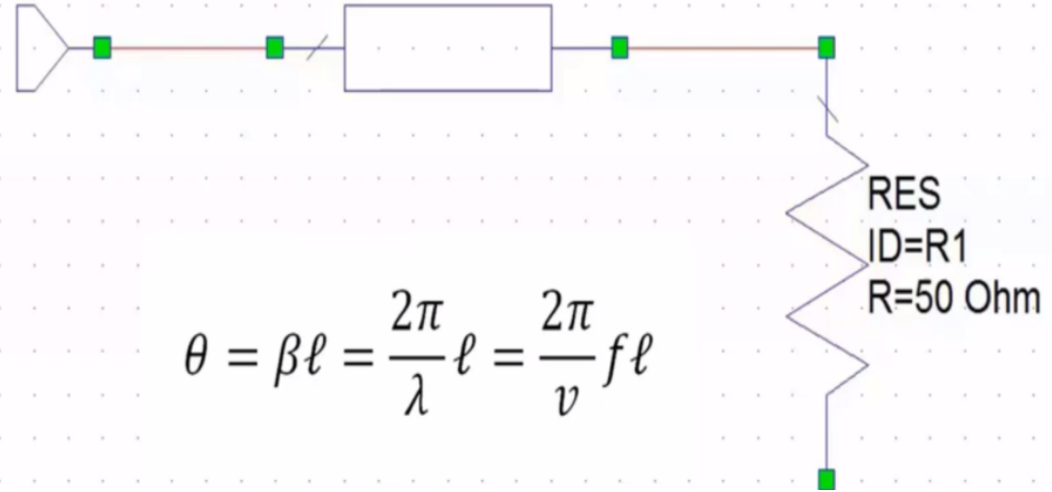TLIN
ID=TL1
Z0=50 Ohm
EI=20 Deg
F0=10000 MHz



EL and the F0 is connected for any F0 there is diffrent EI

$$\theta = \beta \ell = \frac{2\pi}{\lambda} \ell = \frac{2\pi}{v} f \ell$$

Impedance equals to zed which in this

S11 on polar for F0=1Ghz is equall 0 as the port,line,load have 50ohm means max power transfer on 1Ghz

Cange the fonts size from the graph properties and you can copy the graph to other places , this should be tried also the polar limit can be set also to max value 1

tune EI will leads to round move.

