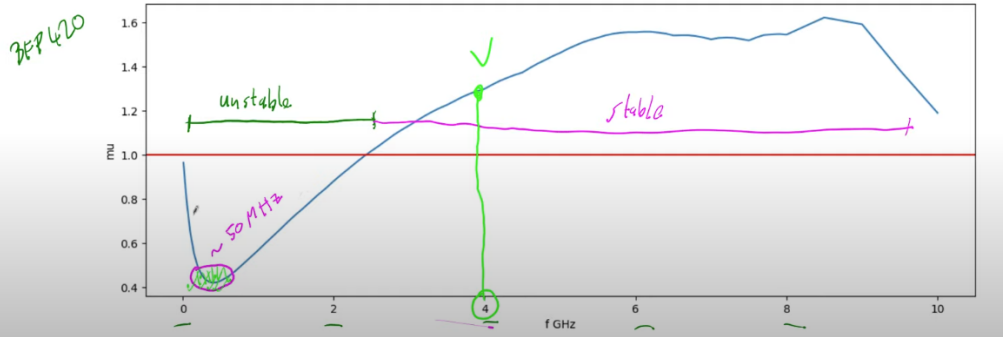


Important Note




It's not sufficient to check the stability at your operating frequency. Oscillations do not care about your design frequency.

They start because they can!



Design for Maximum Gain (Conjugate Matching)

Maximize Gain

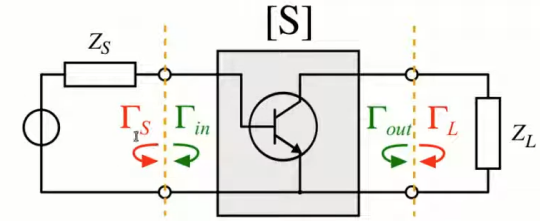

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in}\Gamma_S|^2}, \quad G_0 = |S_{21}|^2, \quad G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

Overall transducer gain is

$$G_T = G_S G_0 G_L$$

- For a given transistor, the gain G_0 is fixed.
- The total gain of the amplifier is then determined by G_L and G_S of the matching sections.
- The maximum gain for

$$\Gamma_{in} = \Gamma_S^*, \quad (22)$$

$$\Gamma_{out} = \Gamma_L^*, \quad (23)$$

Assuming lossless matching sections, the maximum is

$$G_{T_{max}} = \frac{1}{1 - |\Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}. \quad (24)$$